# **Chapter 4: Electric circuits**

## **Knowledge organiser**

#### Charge

An atom has no **charge** because it has equal numbers of positive protons and negative electrons.

When electrons are removed from an atom it becomes positively charged. When electrons are added to an atom it becomes negatively charged.



Insulating materials can become charged when they are rubbed with another insulating material. This is because electrons are transferred from one material to the other. Materials that gain electrons become negatively charged and those that lose electrons

become positively charged. Positive charges do not usually transfer between materials.

Electric charge is measured in coulombs C.

#### Sparks

If two objects have a very strong electric field between them, electrons in the air molecules will be strongly attracted towards the positively charged object. If the electric field is strong enough, electrons will be pulled away from the air molecules and cause a flow of electrons between the two objects - this is a spark.

#### Drawing electric fields

A charged object creates an **electric field** around itself.

If a charged object is placed in the electric field of another charged object it experiences **electrostatic force**. This

means that the two charged objects exert a non-contact force on each other:

- like charges repel each other
- opposing charges attract each other.

The electric field, and the force between two charged objects, gets stronger as the distance between the objects decreases.

### Drawing electric fields

Electric fields can be represented using a diagram with field lines. These show the direction of the force that a small positive charge would experience when placed in the electric field.

When drawing electric fields, make sure:

- field lines meet the surface of charged objects at 90°
- arrows always point away from positive charges and towards negative charges.

#### **Electric current**

**Electric current** is when **charge** flows. The charge in an electric circuit is carried by electrons. The unit of current is the ampere (amp, A).

1 ampere = 1 coulomb of charge flow per second  $Charge(C) = current(A) \times time(s)$ .....

In circuit diagrams, current flows from the positive terminal of a cell or battery to the negative terminal. This is known as conventional current.

In a single closed loop, the current has the same value at any point in the circuit.

Metals are good conductors of electricity because they contain delocalised electrons, which are free to flow through the structure.

#### **Potential difference**

Potential difference (p.d.) is a measure of how much energy is transferred between two points in a circuit. The unit of potential difference is the volt (V).

- The p.d. across a component is the work done on it by each coulomb of charge that passes through it.
- The p.d. across a power supply or battery is the energy transferred to each coulomb of charge that passes through it.

For electrical charge to flow through a circuit there must be a source of potential difference.

Potential difference (V) = energy transferred (J) / charge (C)

() Key terms

#### Make sure you can write a definition for these key terms. ampere charge coulomb current electric field electrostatic force LDR parallel potential difference resistance series static

thermistor

#### Resistance

When electrons move through a circuit, they collide with the ions and atoms of the wires and components in the circuit. This causes resistance to the flow of charge.

The unit of resistance is the ohm  $(\Omega)$ .

A long wire has more resistance than a short wire because electrons collide with more ions as they pass through a longer wire.

The resistance of an electrical component can be found by measuring the current and potential difference:

potential current \_ resistance difference = (Ω) (A) (V) L)

. . . . . . . . . . . . . . . . . . .

#### Circuit components

V = IR



#### **Current-potential difference graphs**

constant.

A graph of current through a component against the p.d. across it (I–V graph), is known as the component characteristic.



filament lamp

The resistance of an ohmic conductor can be found by calculating the gradient at that point and taking the inverse:

resistance =	1 radient.	
		• •







Current is directly proportional to the p.d. in an ohmic conductor at a constant temperature. The resistance is



The current through a diode only flows in one direction called the forward direction. There needs to be a minimum voltage before any current will flow.

As more current flows through the filament, its temperature increases. The atoms in the wire vibrate more, and collide more often with electrons flowing through it, so resistance increases as temperature increases. The resistance of a thermistor decreases and temperature increases. The resistance of a light dependent resistor (LDR) decreases as light intensity increases.

# **Chapter 4: Electric circuits**

## **Retrieval questions**

Learn the answers to the questions below then cover the answers column with a piece of paper and write as many as you can. Check and repeat.

#### P4 questions Answers Put becomes negatively charged by gaining electrons and How does a material become charged? becomes positively charged by losing electrons paper here What will two objects carrying the same type of repel each other charge do if they are brought close to each other? region of space around a charged object in which Put paper What is an electric field? another charged object will experience an electrostatic force . here What happens to the strength of an electric field it decreases as you get further from the charged object? What is electric current? Put paper here rate of flow of charge What units are charge, current, and time coulombs (C), amperes (A), seconds (s) respectively measured in? What is the same at all points when charge flows current in a closed loop? Put paper What must there be in a closed circuit so that source of potential difference (p.d.) electrical charge can flow? nere Which two factors does current depend on and resistance in ohms $(\Omega)$ , p.d. in volts (V)what are their units? Put paper here What happens to the current if the resistance is **1**0 current decreases increased but the p.d. stays the same? conductor where current is directly proportional to What is an ohmic conductor? the voltage so resistance is constant (at constant temperature) Put paper here What happens to the resistance of a filament lamp resistance increases as its temperature increases? What happens to the resistance of a thermistor as 13 resistance decreases its temperature increases? What happens to the resistance of a light-dependent 14 Put paper here resistance decreases resistor when light intensity increases? same current through each component, total p.d. of power supply is shared between components, total **1**5 What are the main features of a series circuit? resistance of all components is the sum of the resistance of each component Put paper here p.d. across each branch is the same, total current through circuit is the sum of the currents in each 16 What are the main features of a parallel circuit? branch - total resistance of all resistors is less than the resistance of the smallest individual resistor